


Design of an External Current Measurement PCB for SiC Inverters

Kaan Ilhan

Technische Universität München

Chair of High-Power Converter Systems

06. August 2025

 

Uhrenturm der TUM


Agenda



 
- 1) Introduction & Motivation
- 2) Design of the Analog Current Measurement PCB
 - a) Revision 1
 - b) Revision 2
- 3) Sensor Technologies & Portfolio
- 4) Experimental Evaluation
 - a) DC Accuracy & Linearity
 - b) Noise & Frequency Behavior
 - c) AC Impedance Characterization
- 5) Conclusion

Introduction & Motivation

- Accurate current sensing is critical in power electronics for control, protection, and efficiency.
- The rise of SiC and GaN semiconductors demands faster and more precise measurement.
- **Focus:** Accurate current sensing for high-current **three-phase SiC inverter** for motor drive.
Suitability of current sensing in real-world




Current Sensing Approaches

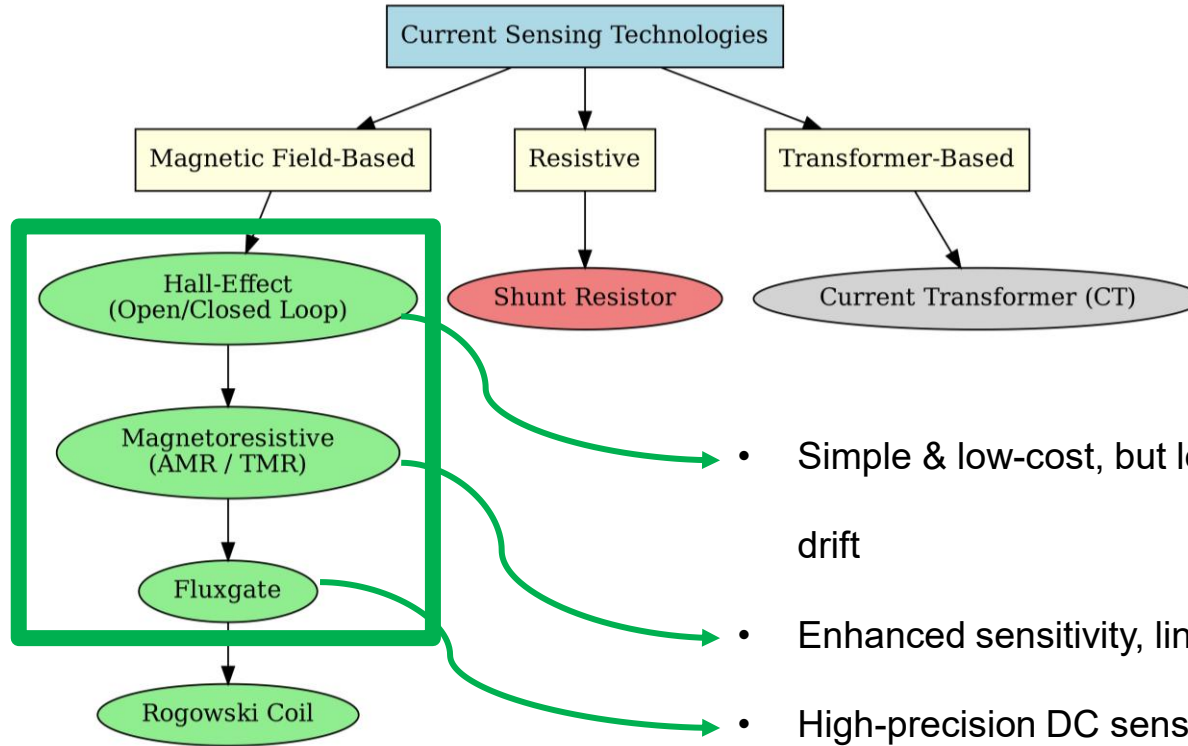

- Simple & low-cost, but lower accuracy and more drift
- Enhanced sensitivity, linearity, and lower noise
- High-precision DC sensing, but introduces modulation ripple


Sensor Topologies: Open-loop vs Closed-loop

Open-loop

 

- Direct sensing
- Limited accuracy




Closed-loop (compensated)

 

- Feedback coil
- Zero-flux

Current Measurement PCB Overview

- 4-layer PCB for analog current measurements with 4 channels
- Input Current: up to $57 A_{RMS}$ / $80 A_{peak}$
- Supports sensors with THD-8 footprint (Sensitec CAS5000, LEM CASR etc.)
- Compatible with UltraZohm platform (RJ45 differential output)
- Thermal safe limit: $100\text{ }^{\circ}\text{C}$ at 80 A continuous current (tested)
- $V_{OCM} = 2.5\text{ V}$
- Supply: $9\text{--}48\text{ V}$ input, step-down to 5.12 VCC+ (adjusted for full-scale swing)
- Phase-to-phase clearance/creepage: 2.5 mm → maximum 500 V_{RMS}

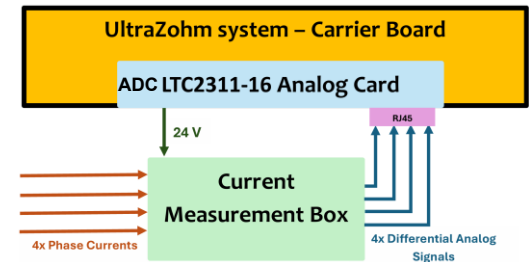  

Current Measurement PCB/Box



Experimental Evaluation 1


DC Measurement: Methodology

- DC sweep to measure differential output voltage ($V_{OUT+} - V_{OUT-}$)
- Measurement taken at RJ45 differential output (after op-amp stage)
- Linear fit applied to extract measured gain and offset

Sensors:

 - 1) LEM CASR series: closed-loop Fluxgate
- 2) Sensitec/Sinomags 5000 series: closed-loop TMR

Sinomags STB-6 (TMR). $I_N = 6 A_{RMS}$ (Range: $\pm 20 A$)



$$\Rightarrow G_{\text{expected}} = \text{OpAmp Gain} \cdot \text{Sensor Sensitivity} = 2 \cdot 104.2 \frac{\text{mV}}{\text{A}} = 208.4 \frac{\text{mV}}{\text{A}}$$

$$\Rightarrow G_{\text{measured}} = 207.6 \frac{\text{mV}}{\text{A}} \quad \Rightarrow \quad \text{Relative Error} = 0.38 \%$$

Experimental Evaluation 2

Time & Frequency Domain Observations: Methodology


- Sinusoidal current input: $1 A_{RMS}$ @ 500 Hz
- Single ended voltage probes for sensor outputs of closed-loop TMR (25 A) and Fluxgate sensors (25 A)
- If needed: Each output waveform is normalized by Gain → **normalized current-equivalent outputs**
- FFT analysis to identify: internal modulation tones (spikes), noise floor (broadband interference), whole spectral content
- Sensor bandwidth (300 kHz & 400 kHz) impacts:
 - a. ripple suppression ability
 - b. Signal fidelity
 - c. Passing through more high-frequency noise

Experimental Evaluation 2

Time & Frequency Domain Observations

- Closed-loop TMR (25 A):** Slightly elevated noise floor. But overall flatter frequency spectrum with no internal modulation spikes.
 - smoother and less noisy time-domain output waveform
- Closed-loop Fluxgate (25 A):** higher ripple due to dominant internal excitation peak at ~435 kHz, as documented in datasheet
- Closed-loop TMR (25 A):** using Micsig optical isolated differential probes connected at the ethernet output, with differential output filter ($f_{cut-off} = 273 \text{ kHz}$)

Frequency Domain

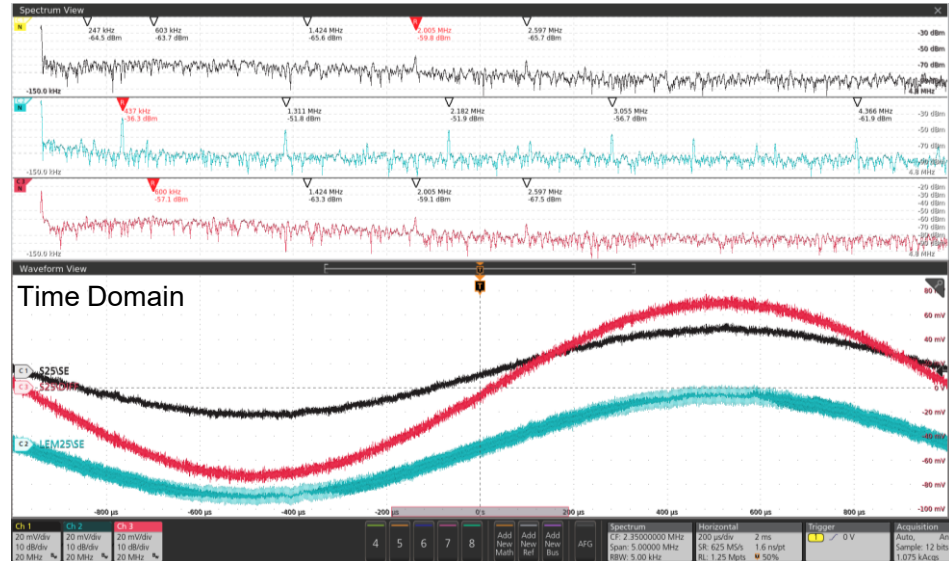

Experimental Evaluation 3


AC Impedance Measurement: Methodology

- Purpose: Evaluate dynamic impedance of sensor output stage across frequency sweep (100 Hz – 10 Mhz)
- Equipment: Bode 100 VNA, APS 1000 amplifier, probes
- Input: 1.175 A_{RMS} sinusoidal current
- Impedance calculated via CH1 (current), CH2 (voltage):


$$Z(f) = \frac{V_{\text{out}}(f)}{I_{\text{in}}(f)} = \frac{V_{\text{CH2}}(f)}{V_{\text{CH1}}(f)}$$

- Measurement limit: Reliable up to **~50 kHz** due to APS 1000 amplifier output drop-off

Test Setup [29]

 

Test setup

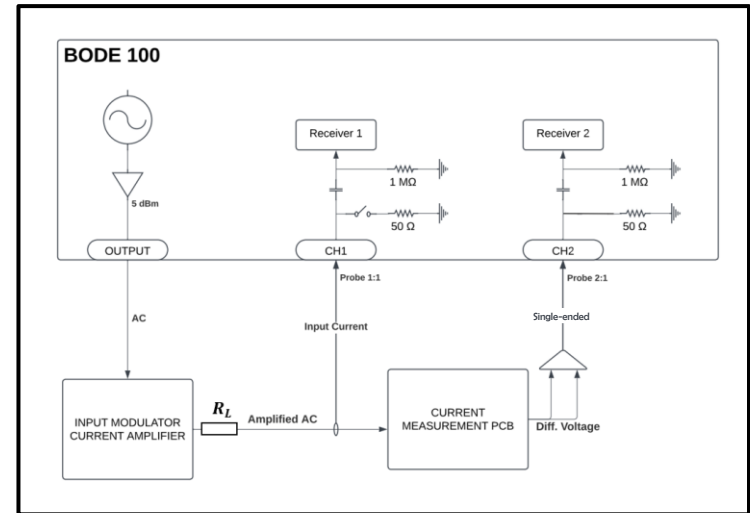

Experimental Evaluation 3

AC Impedance Measurement: Results

- Initial impedance (at 100 Hz) aligns with G_{meas} , measured in DC test ($G_{err} = 0.82\%$ and $G_{err} = 1.25\%$).
- Overall flat and stable impedance response for both sensors
- Slightly flatter magnitude and phase response for **Closed-loop Fluxgate**
- The phase response remains flat below 20 kHz and gradually drops approaching 50 kHz.
- Distinct rise near 2 kHz in **Closed-loop TMR** sensor:
 - due to internal operating transition (field-sensor-controlled operation to transformer-like behavior)

 


Fig. 7: Bode diagram showing impedance magnitude and phase response of tested sensors under a sinusoidal current input of 1.175 A_{RMS}.

Research Internship

- Designed and validated a differential analog current measurement PCB for isolated three-phase sensing
- Integrated within UltraZohm system and ADC interface
- Developed a AC + DC test setup
- Performed full characterization of closed-loop TMR and Fluxgate sensors

Seminar

- Evaluated DC accuracy, time- and frequency response and dynamic behavior of multiple magnetic field-based sensor types (Hall-effect, open-loop AMR, open-loop TMR, closed-loop TMR).


A Comparative Study of Magnetic Current Sensor Technologies with Experimental Evaluation Across Time, Frequency and Impedance Domains

Kaan Ilhan

Technische Universität München

Chair of High-Power Converter Systems

25. July 2025

 

Current Measurement PCB – Rev2

- 4-layer PCB for analog current measurements with 4 channels
- Up to 130 A DC continuous current
- Supports sensors with THD-10 footprint (Sensitec CAS5000, LEM CASR etc.)
- Compatible with UltraZohm platform (RJ45 differential output)
- $V_{OCM} = 2.5\text{ V}$
- Thermal safe limit: 100 °C at 120 A (tested)
- Phase-to-phase clearance/creepage: 9 mm/10mm
 - Maximum phase-to-phase: 1000 V_{RMS} (compliant with IEC 60664-1)
- Redesigned power supply with integrated buck module:
 - reduced EMI resulting from 300 kHz switching noise;
 - output current increased to 1 A based on sensor load


 



Fig. 4: 3D layout view of the custom 4-layer current measurement PCB with color highlighted key blocks: Current input terminals (red), Sensitec sensors (black), differential amplifiers (yellow), power supply circuitry (purple) and Ethernet signal outputs (green).

 

– Rev 1 –

Sinusoidal current input: $1 A_{RMS}$ @ 500 Hz

LEM CASR 6
(Fluxgate)

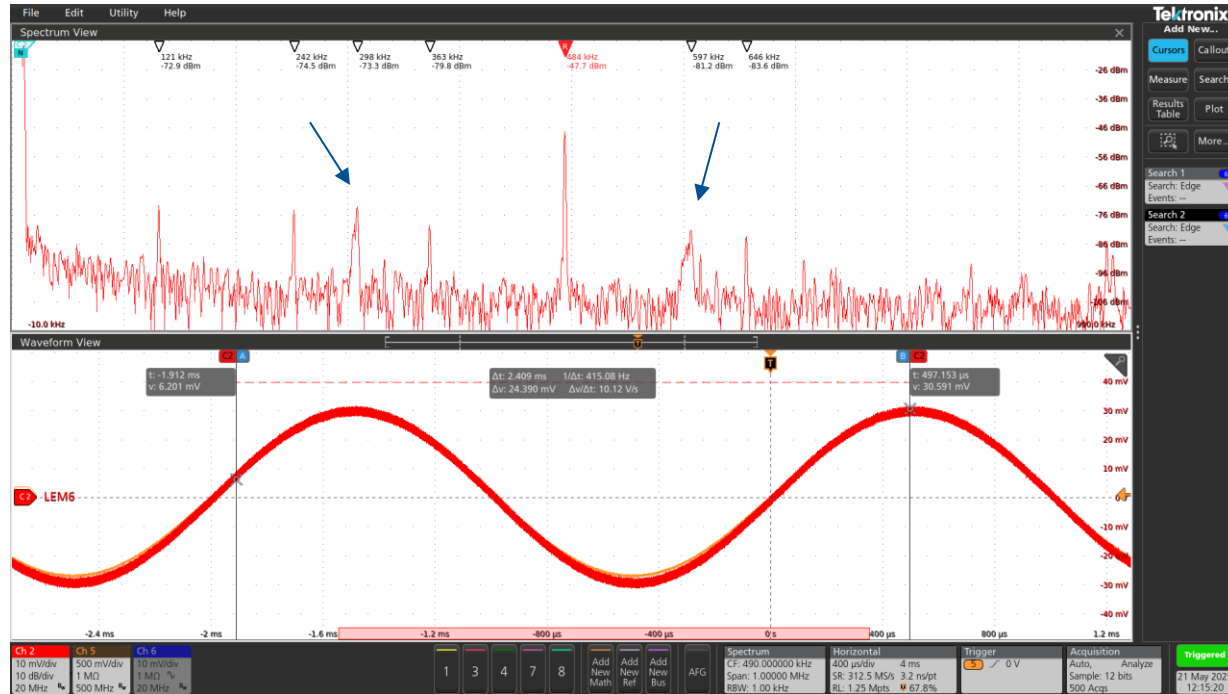


Current Measurement PCB

– Rev1 –



– Rev2 –

 

Sensor Portfolio

- Purpose: to evaluate their performance and compare the actual performance vs datasheet.
 - 1) DC output characterization
 - 2) Time- and frequency domain observation
 - 3) AC impedance measurement.


| | | Datasheet | | | | |
|---|--|---------------|---------------|---|--------------------------|------|
| Sensor | | I_{nom} (A) | f_{BW} (Hz) | I_{ND} ($\mu\text{A}/\sqrt{\text{Hz}}$) | $G_{theoretical}$ (mV/A) | |
| Open-Loop Hall-Effect Sensors (Allegro). Package: SOICW-16 | | | | | | |
| With Evaluation Board | ACS37002LMABTR-050B5-M | ± 50 | 400k | 350 | 40.0 | |
| | ACS37002LMCATR-090B5 | ± 90 | 400k | 350 | 22.2 | |
| | Open-Loop AMR Sensors (Aceinna). Package: SOICW-16 | | | | | |
| | MCA1101-5-5 | ± 5 | 1.5M | 10 | 350.0 | |
| | MCA1101-20-5 | ± 20 | 1.5M | 10 | 90.0 | |
| | MCA1101-50-5 | ± 50 | 1.5M | 10 | 35.0 | |
| | Open-Loop TMR Sensor (Allegro). Package: SOICW-16 | | | | | |
| | CT432-HSWF50MR | ± 50 | 1M | 44.3 | 40.0 | |
| | Closed-Loop TMR Sensors (Sensitec). Package: THD-8 (KH) | | | | | |
| | With Custom PCB (Rev 2) | CAS5050SRA-KH | ± 50 | 400k | N/A | 12.5 |
| CAS5075KRA-KH | | ± 75 | 400k | N/A | 6.25 | |

Experimental Evaluation 1

DC Measurement: Methodology & Metrics

- DC sweep to measure sensors' linear voltage response
- Metrics: **Gain error**, **Linearity error**, **Offset error**
- Reference: Manufacturer datasheet vs. measured output
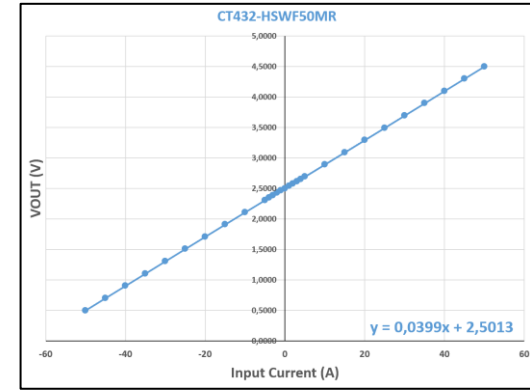
$$V_{\text{out}} = G \cdot I_{\text{in}} + b$$



$$\varepsilon_{\text{acc}} = \underbrace{\left| \frac{G_{\text{measured}} - G_{\text{theoretical}}}{G_{\text{theoretical}}} \right| \times 100\%}_{\text{Gain error}} + \underbrace{|r|}_{\text{Linearity error}} + \underbrace{\left| \frac{b - V_{\text{ref}}}{y_{\text{FS}}} \right| \times 100\%}_{\text{Offset error}}$$

$$r = \pm \frac{\Delta L_{\text{max}}}{y_{\text{FS}}} \times 100\%$$

$$y_{\text{FS}} = G_{\text{meas}} \cdot I_{\text{N}}$$

| Sensor | Datasheet | | | Measured/Calculated | | | | |
|---|----------------------|--------------------------|---------------------------------|------------------------------|--------|------------------------|--------|----------------------|
| | f _{BW} (Hz) | I _{ND} (μA/√Hz) | G _{theoretical} (mV/A) | G _{measured} (mV/A) | b (V) | ΔL _{max} (mV) | r (%) | ε _{acc} (%) |
| Open-Loop Hall-Effect Sensors (Allegro). Package: SOICW-16 | | | | | | | | |
| ACS37002LMABTR-050B5-M | 400k | 350 | 40.0 | 36.1 | 2.502 | 8.3 @ -35 A | 0.23 | 11.63 |
| ACS37002LMCATR-090B5 | 400k | 350 | 22.2 | 21.7 | 2.4999 | 5.4 @ -3 A | 0.138 | 3.08 |
| Open-Loop AMR Sensors (Accina). Package: SOICW-16 | | | | | | | | |
| MCA1101-5-5 | 1.5M | 10 | 350.0 | 333.4 | 2.1983 | -91.0 @ -4 A | -2.73 | 7.50 |
| MCA1101-20-5 | 1.5M | 10 | 90.0 | 89.6 | 2.1796 | -13.6 @ -2 A | -0.38 | 1.06 |
| MCA1101-50-5 | 1.5M | 10 | 35.0 | 34.7 | 2.1777 | 42.7 @ 50 A | 1.23 | 2.37 |
| Open-Loop TMR Sensor (Allegro). Package: SOICW-16 | | | | | | | | |
| CT432-HSWF50MR | 1M | 44.3 | 40.0 | 39.9 | 2.501 | 7.9 @ 4 A | 0.198 | 0.52 |
| Closed-Loop TMR Sensors (Sensitec). Package: THD-8 (KH) | | | | | | | | |
| CAS5050SRA-KH | 400k | N/A | 12.5 | 12.5 | 2.4933 | -1.7 @ 50 A | -0.136 | 0.32 |
| CAS5075KRA-KH | 400k | N/A | 6.25 | 6.22 | 2.501 | -1.7 @ 75 A | -0.182 | 0.35 |

Experimental Evaluation 1

DC Measurement: Results

- Closed-loop TMR sensors: best accuracy ($\epsilon_{acc} < 0.35\%$)
- Open-loop Hall sensors: highest error (ϵ_{acc} up to 11%)
- AMR sensors: good gain, but gain & linearity issues in lower range variant
- Open-loop TMR: excellent overall accuracy ($\epsilon_{acc} \sim 0.5\%$) despite simplicity
- Closed-loop + MR technology = best trade-off in precision & stability

$$\epsilon_{acc} = \underbrace{\left| \frac{G_{measured} - G_{theoretical}}{G_{theoretical}} \right| \times 100\%}_{\text{Gain error}} + \underbrace{|r|}_{\text{Linearity error}} + \underbrace{\left| \frac{b - V_{ref}}{y_{FS}} \right| \times 100\%}_{\text{Offset error}}$$

| Sensor | Datasheet | | | Measured/Calculated | | | | | |
|---|---------------|--------------------------------|--------------------------|-----------------------|---------|-----------------------|---------|----------------------|--|
| | f_{BW} (Hz) | I_{ND} ($\mu A/\sqrt{Hz}$) | $G_{theoretical}$ (mV/A) | $G_{measured}$ (mV/A) | b (V) | ΔL_{max} (mV) | r (%) | ϵ_{acc} (%) | |
| Open-Loop Hall-Effect Sensors (Allegro). Package: SOICW-16 | | | | | | | | | |
| ACS37002LMABTR-050B5-M | 400k | 350 | 40.0 | 36.1 | 2.502 | 8.3 @ -35 A | 0.23 | 11.63 | |
| ACS37002LMCATR-090B5 | 400k | 350 | 22.2 | 21.7 | 2.4999 | 5.4 @ -3 A | 0.138 | 3.08 | |
| Open-Loop AMR Sensors (Aceinna). Package: SOICW-16 | | | | | | | | | |
| MCA1101-5-5 | 1.5M | 10 | 350.0 | 333.4 | 2.1983 | -91.0 @ -4 A | -2.73 | 7.50 | |
| MCA1101-20-5 | 1.5M | 10 | 90.0 | 89.6 | 2.1796 | -13.6 @ -2 A | -0.38 | 1.06 | |
| MCA1101-50-5 | 1.5M | 10 | 35.0 | 34.7 | 2.1777 | 42.7 @ 50 A | 1.23 | 2.37 | |
| Open-Loop TMR Sensor (Allegro). Package: SOICW-16 | | | | | | | | | |
| CT432-HSWF50MR | 1M | 44.3 | 40.0 | 39.9 | 2.501 | 7.9 @ 4 A | 0.198 | 0.52 | |
| Closed-Loop TMR Sensors (Sensitec). Package: THD-8 (KH) | | | | | | | | | |
| CAS5050SRA-KH | 400k | N/A | 12.5 | 12.5 | 2.4933 | -1.7 @ 50 A | -0.136 | 0.32 | |
| CAS5075KRA-KH | 400k | N/A | 6.25 | 6.22 | 2.501 | -1.7 @ 75 A | -0.182 | 0.35 | |

Experimental Evaluation 2



Time & Frequency Domain Observations: Methodology

- Sinusoidal current input: $0.5 A_{RMS}$ @ 1 kHz
- Single ended probes for sensor voltage outputs
- Each output waveform is normalized by Gain → **normalized current-equivalent outputs**
- FFT analysis identifies: Internal modulation tones (spikes), noise floor (broadband interference), spectral content...
- Sensor bandwidth impacts:
 - a. ripple suppression ability
 - b. Signal fidelity
 - c. Passing through more high-frequency noise

Experimental Evaluation 2

Time & Frequency Domain Observations

Time Domain

Frequency Domain

- **Open-loop AMR** & **Open-loop TMR**: Best signal clarity
lowest ripple, flattest FFT noise. Minimal spectral content.
- **Closed-loop TMR (50A)**: moderate ripple; slightly elevated noise floor. Low broadband noise
- **Closed-loop TMR (75A)**: highest ripple due to elevated noise floor
- **Hall-Effect**: Both with high ripple due to elevated noise floor and dominant internal modulation spike at ~973 kHz

Open-loop TMR


Hall-effect

Open-loop AMR

Closed-loop
TMR

Hall-effect

Closed-loop
TMR

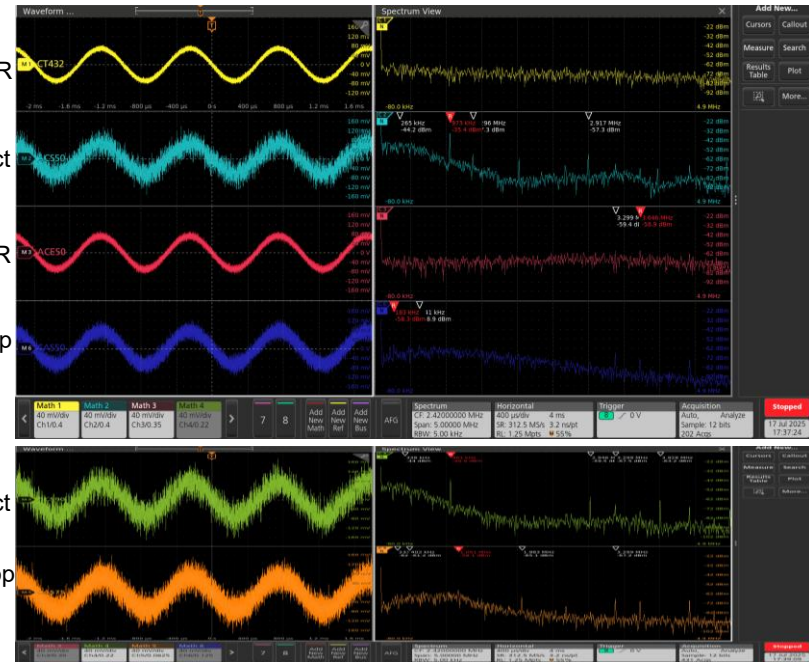

➔ FFT vs. datasheet noise: no direct correlation!
Lowest noise density (I_{ND}) sensors did not necessarily show better performance

Experimental Evaluation 3


AC Impedance Measurement: Methodology

- Purpose: Evaluate dynamic impedance of sensor output stage across frequency sweep (10 Hz – 10 Mhz)
- Equipment: Bode 100 VNA, APS 1000 amplifier, probes
- Input: $1.175 A_{RMS}$ sinusoidal current
- Impedance calculated via CH1 (current), CH2 (voltage):


$$Z(f) = \frac{V_{out}(f)}{I_{in}(f)} = \frac{V_{CH2}(f)}{V_{CH1}(f)}$$

- Measurement limit: Reliable up to **~50 kHz** due to APS 1000 amplifier output drop-off

Test Setup [29]

 

Test setup

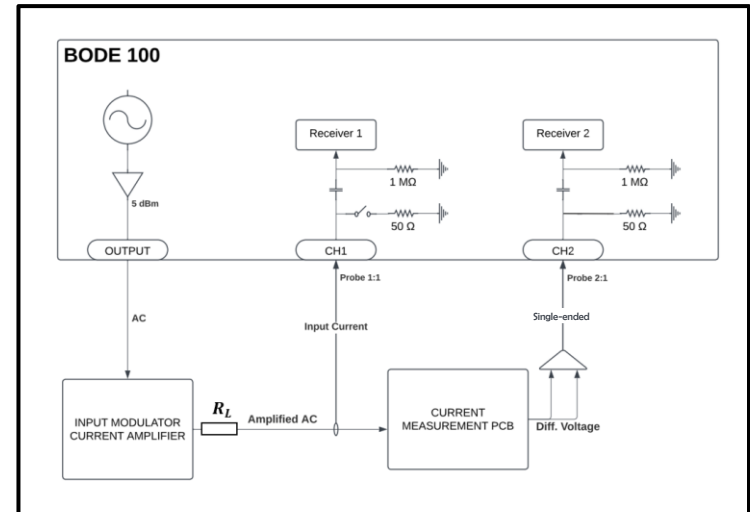

Experimental Evaluation 3

AC Impedance Measurement: Results

- Initial impedance (at 10 Hz) aligns with G_{meas} , measured in DC test.
- Flat and stable impedance response for **Open-loop TMR** and **Open-loop AMR** sensors
- Sharp zigzag fluctuations for **Hall-Effect** sensors: indicates internal frequency-dependent Gain changes.
- Distinct dip near 2 kHz for both **Closed-loop TMR** sensors:
→ due to internal operating transition (field-sensor-controlled operation to transformer-like behavior)

 


Fig. 7: Bode diagram showing impedance magnitude and phase response of tested sensors under a sinusoidal current input of 1.175 A_{RMS}.

Conclusion

- Hall-effect sensors:
 - Poor gain precision
 - High thermal drift under static load
 - High broadband noise + modulation tones → High ripple
- AMR & open-loop TMR sensors:
 - Lowest noise, flat FFT → minimal ripple
- AC impedance:
 - AMR & TMR = most stable dynamic behavior
- **Variants matter:**
 - Closed-loop TMR models from same brand (Sensitec) showed different results
- AMR & TMR suitable for high-current, fast-switching inverters (e.g. SiC inverters)

References



- [1] P. Niklaus, D. Bortis, and J. W. Kolar, “High-Bandwidth High-CMRR Current Measurement for a 4.8 MHz Multi-Level GaN Inverter AC Power Source,” APEC, 2021.
- [2] Allegro Microsystems, “From Hall Effect to TMR: A Comparison of Magnetic Sensing Technologies,” AN117, 2023.
- [3] Allegro Microsystems, “Achieving Closed-Loop Accuracy in Open-Loop Current Sensors,” 2023.
- [4] B. Mammano, Current Sensing Solutions for Power Supply Designers, TI Seminar SEM1200, SLUP114, 1997.
- [5] H. Kirkham, “Current Measurement Methods for the Smart Grid,” IEEE Power Engineering Society General Meeting, 2009.
- [6] S. C. Mukhopadhyay and R. Y. M. Huang, Sensors, Springer, 2008, pp. 23–43.
- [7] H. Deng et al., “High Precision Closed-loop TMR Current Sensor for Small Current Measurement,” IAECST, 2023.
- [8] Allegro Microsystems, CT432: XtremeSense TMR Current Sensor, Rev. 2, Nov. 2023.
- [9] Allegro Microsystems, ACS37002: Hall Effect Current Sensor IC, Rev. 1.0, 2021.
- [10] Allegro Microsystems, ACSEVB-MC16 Evaluation Board User Guide, Aug. 2023.
- [11] ACEINNA Inc., MCx1101 EVB User Manual, v1.3, 2021. Available: aceinna.com
- [12] ACEINNA, MCA1101-xx-5 Datasheet, Rev. L, June 2024.
- [13] Sensitec GmbH, CAS5000-Series Datasheet, Rev. 02/2022.
- [14] Würth Elektronik eiSos GmbH, 7461001 Terminal Datasheet, v3.0, June 2023.
- [15] Texas Instruments, THS4521 Amplifier Datasheet, Rev. G, July 2023.
- [16] Texas Instruments, REF35250 Voltage Reference, Rev. D, Oct. 2023.
- [17] Texas Instruments, TPSM365R3 Power Module, Rev. A, June 2024.
- [18] Texas Instruments, TPS7A47 LDO Regulator, Rev. I, Apr. 2023.
- [19] IEC 60664-1, Insulation Coordination for Equipment, May 2020.
- [20] IEC 61800-5-1, Adjustable Speed Drive Systems Safety, Aug. 2022.
- [21] IPC-9592B, Power Conversion Device Requirements, Jan. 2013.
- [22] IPC-2221B, Standard on PCB Design, Nov. 2012.
- [23] W. Zhang and T. LaBella, “Demystifying Clearance and Creepage,” TI Power Supply Design Seminar, SLUP419, 2024.
- [24] M. Lei et al., “TMR Sensor with Temperature Compensation,” Energy Reports, vol. 8, pp. 137–146, 2022.
- [25] M. Cerna and A. F. Harvey, “Fundamentals of FFT-Based Signal Analysis,” NI App Note 041, 2000.
- [26] Spitzenberger & Spies, APS 1000 Amplifier Overview, Rev. 1107-e-0008-1.
- [27] B. Zhang, “Time-delay Compensation Techniques,” PEMC Conference, 2015.
- [28] Anup Bhalla, “Practical considerations when comparing SiC and GaN in power applications,” *Elektronica-Plus*, July 17, 2018. [Online]. Available: https://elektronica-plus.it/practical-considerations-when-comparing-sic-and-gan-in-power-applications_96479/. [Accessed: Jul. 22, 2025].
- [29] OMICRON Lab, *Bode Analyzer Suite - User Manual*, Rev. 3.5. OMICRON electronics GmbH, Austria, 2022. [Online]. Available: <https://www.omicron-lab.com/fileadmin/assets/Bode-Analyzer-Suite/Documents/Bode-Analyzer-User-Manual.pdf>. [Accessed: Jul. 22, 2025].